# **Station Directions**

Station 1: Rice/Beans with Speaker

- 1. Turn on the speaker.
- 2. Observe what happens to the rice/beans.
- 3. Review and discuss with a partner the prompts on the Energy Transformation Data Sheet for Station 1.
- 4. Write your answers in your science notebook or on the data sheet.



### Resource

# **Station Directions**

Station 2: Circuit with Motor and Battery

- 1. Connect the battery with the wires and motor. Hold the wires from the motor onto both ends of the battery.
- 2. Observe what happens to the motor.
- 3. Review and discuss with a partner the prompts on the Energy Transformation Data Sheet for Station 2.
- 4. Write your answers in your science notebook or on the data sheet.

### Resource

# **Station Directions**

Station 3: Circuit with Buzzer and Solar Panel

- 1. Connect the solar panel with the wires and buzzer.
- 2. Observe what happens to the buzzer.
- 3. Review and discuss with a partner the prompts on the Energy Transformation Data Sheet for Station 3.
- 4. Write your answers in your science notebook or on the data sheet.

### Resource

## **Station Directions**

Station 4: Circuit with Light Bulb and Hand Generator

- 1. Connect the hand generator with wire and light bulb.
- 2. Turn the generator.
- 3. Observe what happens to the light bulb.
- 4. Review and discuss with a partner the prompts on the Energy Transformation Data Sheet for Station 4.
- 5. Write your answers in your science notebook or on the data sheet.